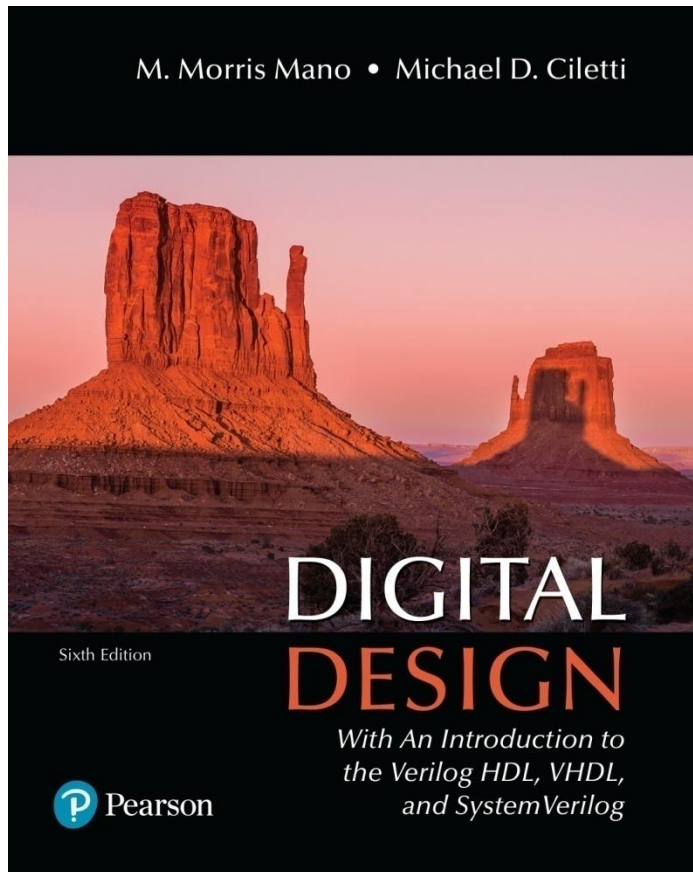


Digital Design


With an Introduction to the Verilog HDL, VHDL, and SystemVerilog

6th Edition




Chapter 03 Gate-Level Minimization

Figure 3.1 Two-variable K-map.

 


(a)

 


(b)

Figure 3.2
Representation of functions in the K-map.

 

(a) xy

 

(b) $x + y$

Figure 3.3
Three-variable K-map.

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6

(a)

		y			
		yz			
		00	01	11	10
x	0	m_0 $x'y'z'$	m_1 $x'y'z$	m_3 $x'yz$	m_2 $x'yz'$
	1	m_4 $xy'z'$	m_5 $xy'z$	m_7 xyz	m_6 xyz'
		z			

(b)

Figure 3.4

Map for Example 3.1, $F(x, y, z) = \Sigma (2, 3, 4, 5) = x'y + xy'$.


 


Figure 3.5

 
Map for Example 3.2, $F(x, y, z) = \Sigma (3, 4, 6, 7) = yz + xz'$.



Note: $xy'z' + xyz' = xz'$

Figure 3.6

 Map for Example 3.3, $F(x, y, z) = \Sigma (0, 2, 4, 5, 6) = z' + xy'$.



Note: $y'z' + yz' = z'$

Figure 3.7

Map of Example 3.4, $A'C + A'B + AB'C + BC = C + A'B$.


 


Figure 3.8
Four-variable map.

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6
m_{12}	m_{13}	m_{15}	m_{14}
m_8	m_9	m_{11}	m_{10}


(a)

 

(b)

Figure 3.9

 
Map for Example 3.5, $F(w, x, y, z) = \Sigma (0, 1, 2, 4, 5, 6, 8, 9, 12, 13, 14) = y' + w'z' + xz'$.



Note: $w'y'z' + w'yz' = w'z'$
 $xy'z' + xyz' = xz'$


Figure 3.10

 Map for Example 3.6, $A'B'C' + B'CD' + A'BCD' + AB'C = B'D' + B'C' + A'CD'$.




Note: $A'B'C'D' + A'B'CD' = A'B'D'$
 $AB'C'D' + AB'CD' = AB'D'$
 $A'B'D' + AB'D' = B'D'$
 $A'B'C' + AB'C' = B'C'$

Figure 3.11
Simplification using prime implicants.

 

Note: $A'B'C'D' + A'B'CD' = A'B'D'$
 $AB'C'D' + AB'CD' = AB'D'$
 $A'B'D' + AB'D' = B'D'$

 
(a) Essential prime implicants
 BD and $B'D'$



(b) Prime implicants CD , $B'C$,
 AD , and AB'

Figure 3.12

 Map for Example 3.7, $F(A, B, C, D) = \Sigma (0, 1, 2, 5, 8, 9, 10) = BD + BC + ACD = (A' + B')(C' + D')(B' + D)$.



Note: $BC'D' + BCD' = BD'$

Figure 3.13
Gate implementations of the function of Example 3.7.


 
 


Table 3.1
Truth Table of Function F.

<i>x</i>	<i>y</i>	<i>z</i>	<i>F</i>
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0


Figure 3.14
Map for the function of Table 3.1.

 


Practice Exercise 3.8

<i>wxyz F</i>	<i>wxyz F</i>
0000 1	1000 1
0001 0	1001 0
0010 1	1010 1
0011 0	1011 0
0100 0	1100 1
0101 0	1101 1
0110 0	1110 1
0111 0	1111 0

Figure 3.15
Example with don't-care conditions.

 

(a) $F = yz + w'x'$

 

(b) $F = yz + w'z$

Figure 3.16
Logic operations with NAND gates.



 


Figure 3.17

 Two graphic symbols for a three-input NAND gate.




(a) AND-invert

 


(b) Invert-OR


Figure 3.18
Three ways to implement $F = AB + CD$.

 

(a)



 


(b)

 

(c)

Figure 3.19
Solution to Example 3.9.

   

Practice Exercise 3.10



 


Figure 3.20
Implementing $F = A(CD + B) + BC'$.

 

(a) AND-OR gates

 

(b) NAND gates

Figure 3.21

Implementing $F = (AB' + A'B)(C + D')$.

 
 


Figure 3.22
Logic operations with NOR gates.

 


Figure 3.23
Two graphic symbols for the NOR gate.

 
 


Figure 3.24
Implementing $F = (A + B)(C + D)E$.


 


Figure 3.25
Implementing $F = (AB' + A'B)(C + D')$ with NOR gates.

 

Practice Exercise 3.11


 
 


Figure 3.26

Wired logic


(a) Wired-AND logic with two NAND gates

 (b) Wired-OR in emitter-coupled logic (ECL) gates.



(a) Wired-AND in open-collector
TTL NAND gates.


(AND-OR-INVERT)

 


(b) Wired-OR in ECL gates

(OR-AND-INVERT)


Figure 3.27
AND–OR–INVERT circuits, $F = (AB + CD + E)'$.

 

(a) AND–NOR

 


(b) AND–NOR

 


(c) NAND–AND

Figure 3.28

 
OR–AND–INVERT circuits, $F = [(A + B)(C + D)E]'$.



(a) OR–NAND

 

(b) OR–NAND

 

(c) NOR–OR

Table 3.2

Implementation with Other Two-Level Forms.

Equivalent Nondegenerate Implementation		Implements the Form	Simplify F' into	To Get an Output of
(a)	(b) *			
AND-NOR	NAND-AND	AND-OR-INVERT	Sum-of-products form by combining 0's in the map.	F
OR-NAND	NOR-OR	OR-AND-INVERT	Product-of-sums form by combining 1's in the map and then complementing.	F

*Form (b) requires an inverter for a single literal term.

Figure 3.29

Other two-level implementations.

		y			
		xz			
x	0	00	01	11	10
	1	01	10	11	10
$x'y'z'$	0	m_0	m_1	m_3	m_2
	1	m_4	m_5	m_7	m_6
		z			
		0	1	0	1
		1	0	0	1

$F = x'y'z' + xyz'$
 $F' = x'y + xy' + z$

(a) Map simplification in sum of products



 
 


Figure 3.30
Logic diagrams for exclusive-OR implementations.

 

(a) Exclusive-OR with AND-OR-NOT gates

 

(b) Exclusive-OR with NAND gates

Figure 3.31
Map for a three-variable exclusive-OR function.

$A \backslash BC$		B			
		00	01	11	10
A	0	m_0	m_1 1	m_3	m_2 1
	1	m_4 1	m_5	m_7 1	m_6

C


(a) Odd function $F = A \oplus B \oplus C$

$A \backslash BC$		B			
		00	01	11	10
A	0	m_0 1	m_1	m_3 1	m_2
	1	m_4	m_5 1	m_7	m_6 1


C

(b) Even function $F = (A \oplus B \oplus C)'$

Figure 3.32
Logic diagram of odd and even functions.

 

(a) 3-input odd function

 

(b) 3-input even function

Figure 3.33
Map for a four-variable exclusive-OR function.

AB \ CD		C			
		00	01	11	10
A	00	m_0	m_1 1	m_3	m_2 1
	01	m_4 1	m_5	m_7 1	m_6
	11	m_{12}	m_{13} 1	m_{15}	m_{14} 1
	10	m_8 1	m_9	m_{11} 1	m_{10}
		D			

(a) Odd function $F = A \oplus B \oplus C \oplus D$


AB \ CD		C			
		00	01	11	10
A	00	m_0 1	m_1	m_3 1	m_2
	01	m_4	m_5 1	m_7	m_6 1
	11	m_{12} 1	m_{13}	m_{15} 1	m_{14}
	10	m_8	m_9 1	m_{11}	m_{10} 1
		D			

(b) Even function $F = (A \oplus B \oplus C \oplus D)'$


Table 3.3
Even-Parity-Generator Truth Table.

Three-Bit Message			Parity Bit
<i>x</i>	<i>y</i>	<i>z</i>	<i>P</i>
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Figure 3.34
Logic diagram of a parity generator and checker.

 

(a) 3-bit even-parity generator

 

(b) 4-bit even-parity checker

Table 3.4
Even-Parity-Checker Truth Table.

Four Bits Received				Parity Error Check
<i>x</i>	<i>y</i>	<i>z</i>	<i>P</i>	<i>C</i>
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
0	1	0	0	1
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	0
1	1	0	1	1
1	1	1	0	1
1	1	1	1	0

Figure 3.35

A logic diagram (schematic) for the Boolean equations $D = A + B$ $E = CD$.

 


Figure PE3.12

 


Figure 3.36
Entity-Architecture pair for *or_and_vhdl*.

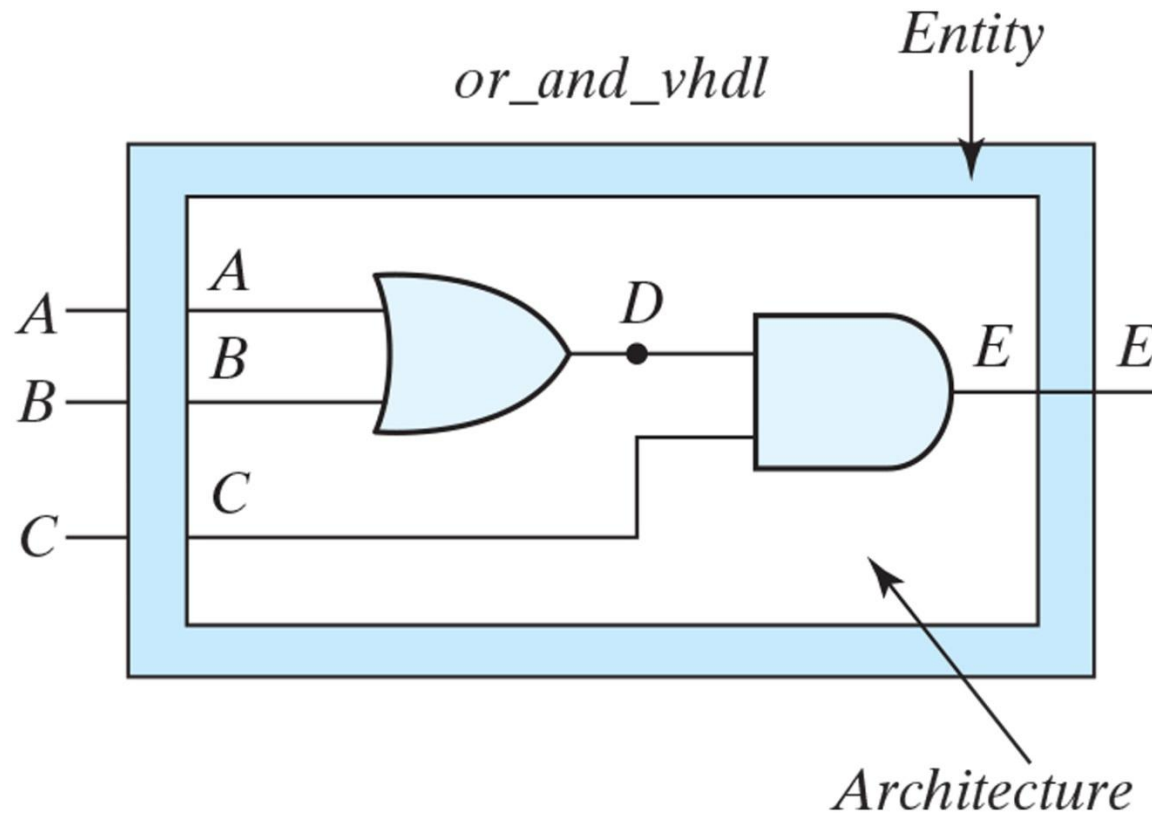


Figure PE3.13

 


Figure 3.37
Schematic for *and_or_prop_delay*.

 


Table 3.5
Output of Gates after Delay.

		Input			Output		
Time Units (ns)		A	B	C	E	w1	D
Initial	—	0	0	0	1	0	1
Change	—	1	1	1	1	0	1
	10	1	1	1	0	0	1
	20	1	1	1	0	0	1
	30	1	1	1	0	1	0
	40	1	1	1	0	1	0
	50	1	1	1	0	1	1

Figure 3.38
Simulation waveforms of *and_or_prop_delay*.

 


Figure 3.39
Entity-architecture for a structural model of *and_or_prop_delay_vhdl*.

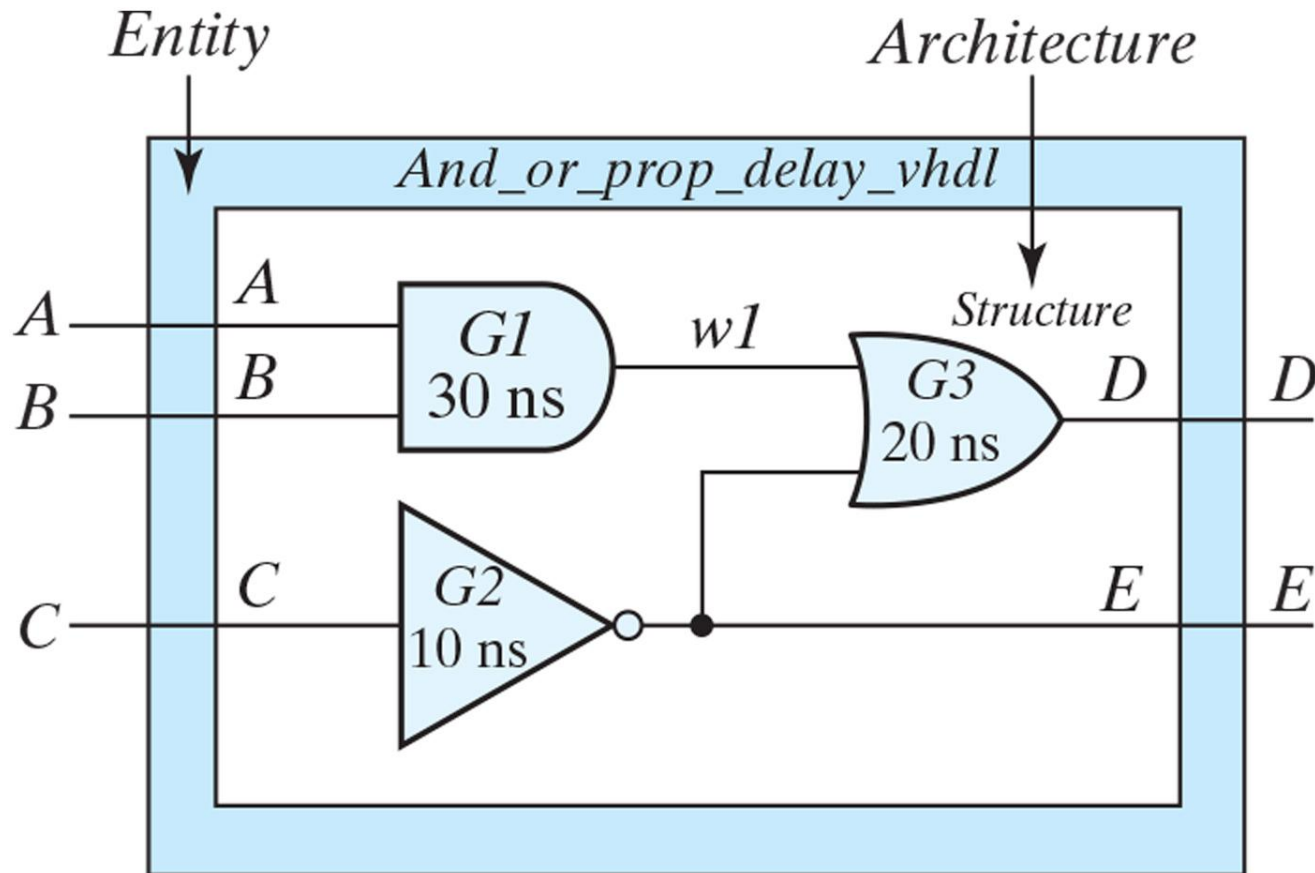


Table 3.6

Logic Symbols of the *IEEE_std_logic_1164* Package.

‘U’	Uninitialized
‘X’	Strong drive, unknown logic value
‘0’	Strong drive, logic 0
‘1’	Strong drive, logic 1
‘Z’	High impedance
‘W’	Weak drive, unknown logic value
‘L’	Weak drive, logic 0
‘H’	Weak drive, logic 1
‘-’	Don’t care

Figure 3.40
Schematic for *Circuit with_UDP_02467*.

 


Figure P3.38

