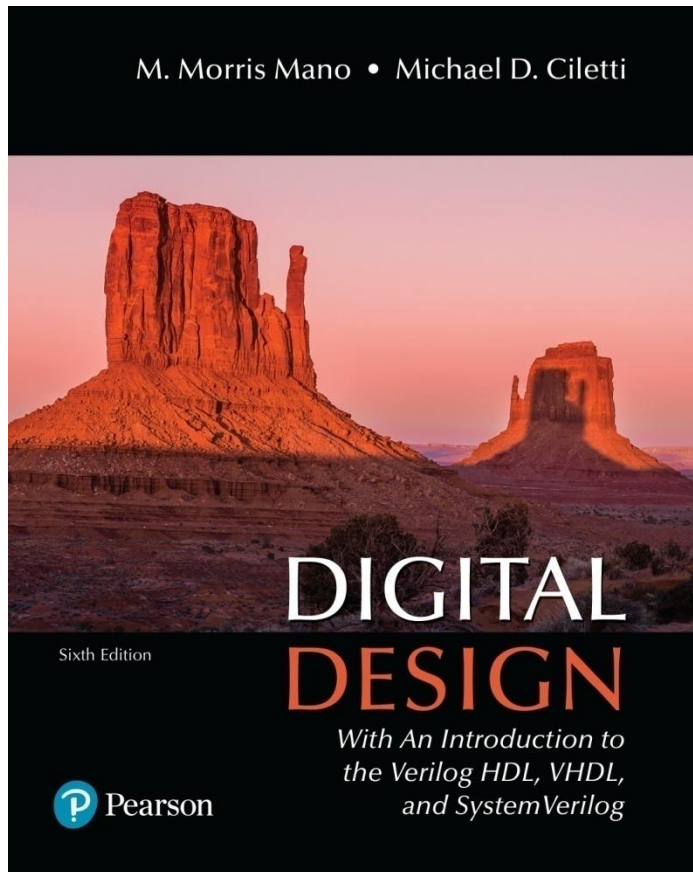


# Digital Design

With an Introduction to the Verilog HDL, VHDL, and SystemVerilog


6<sup>th</sup> Edition




## Chapter 06

### Registers and Counters

**Figure 6.1**  
**Four-bit register.**

 

**Figure 6.2**  
**Four-bit register with parallel load.**

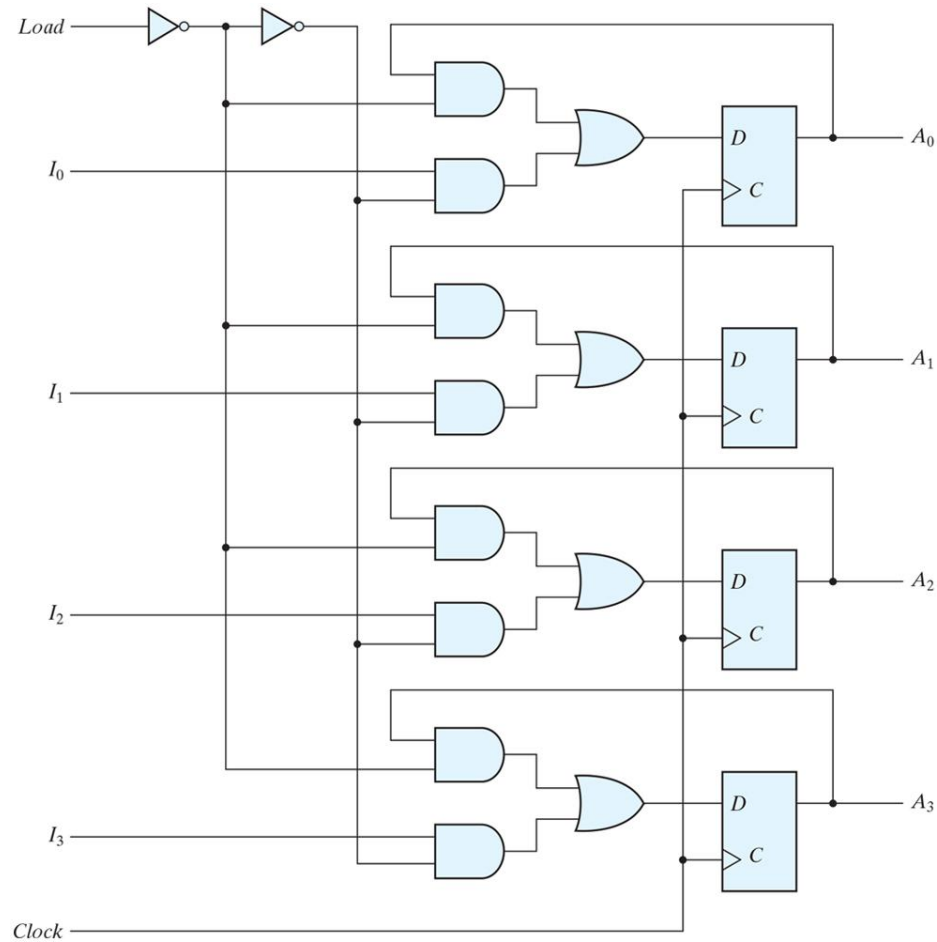

**Figure 6.3**  
**Four-bit shift register.**

 


Figure PE6.1



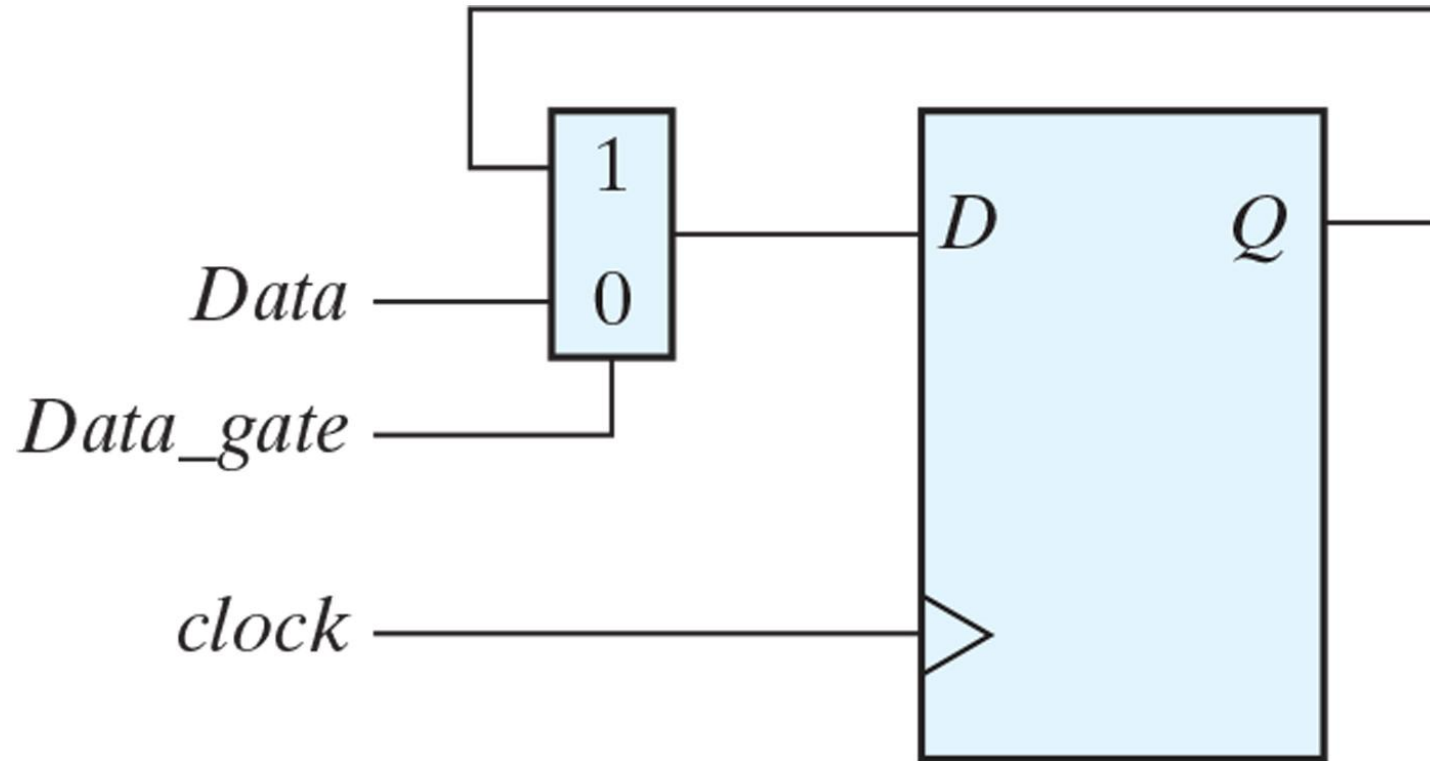


Figure 6.4  
Serial transfer from register A to register B.

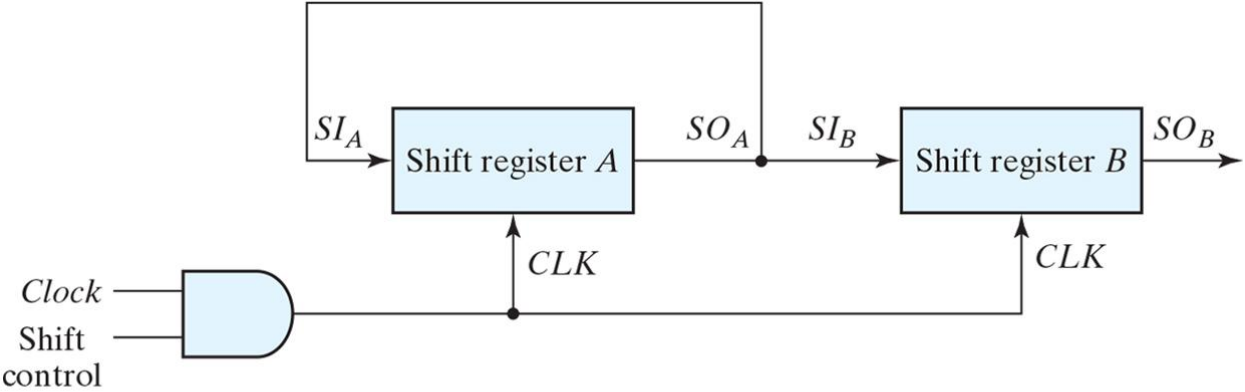

(a) Block diagram

 


(b) Timing diagram

**Table 6.1**  
**Serial-Transfer Example.**

<b>Timing Pulse</b>	<b>Shift Register A</b>				<b>Shift Register B</b>			
Initial value	1	0	1	1	0	0	1	0
After $T_1$	1	1	0	1	1	0	0	1
After $T_2$	1	1	1	0	1	1	0	0
After $T_3$	0	1	1	1	0	1	1	0
After $T_4$	1	0	1	1	1	0	1	1

Figure 6.5  
Serial adder.

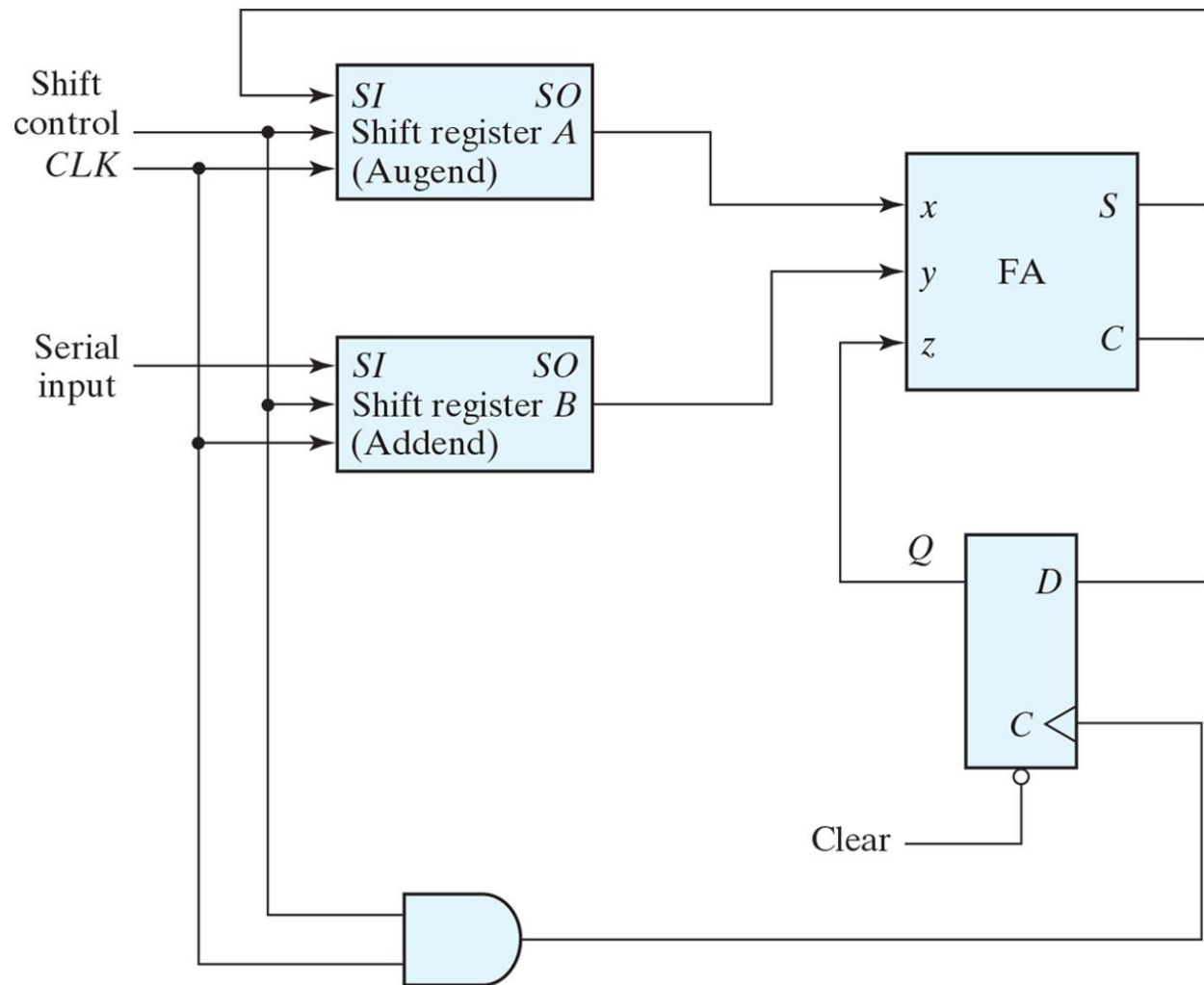





**Table 6.2**  
**State Table for Serial Adder.**

Present State		Inputs		Next State	Output	Flip-Flop Inputs	
$Q$		$x$	$y$	$Q$	$S$	$J_Q$	$K_Q$
0		0	0	0	0	0	X
0		0	1	0	1	0	X
0		1	0	0	1	0	X
0		1	1	1	0	1	X
1		0	0	0	1	X	1
1		0	1	1	0	X	0
1		1	0	1	0	X	0
1		1	1	1	1	X	0

**Figure 6.6**  
**Second form of serial adder.**

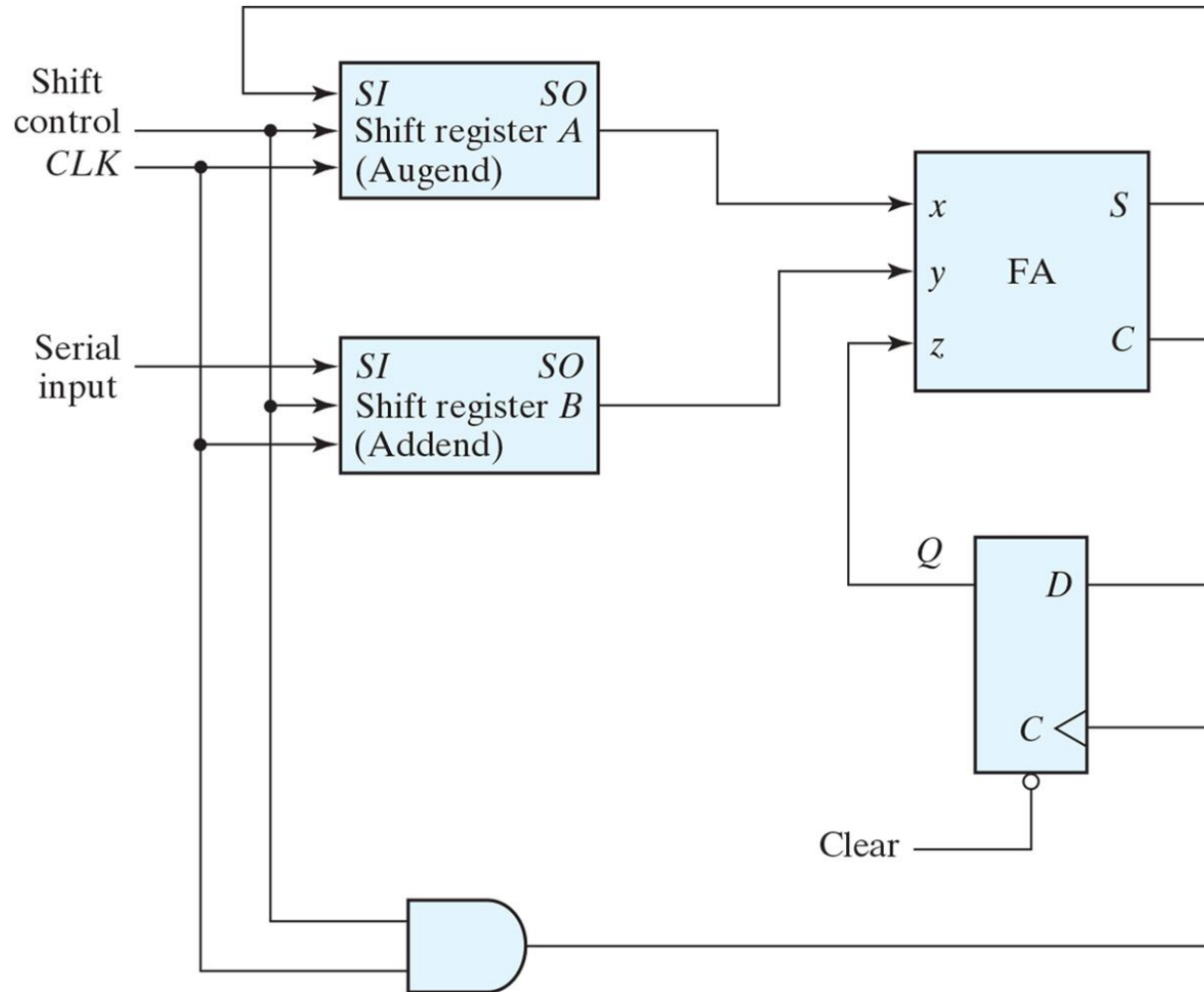

**Figure 6.7**  
**Four-bit universal shift register.**

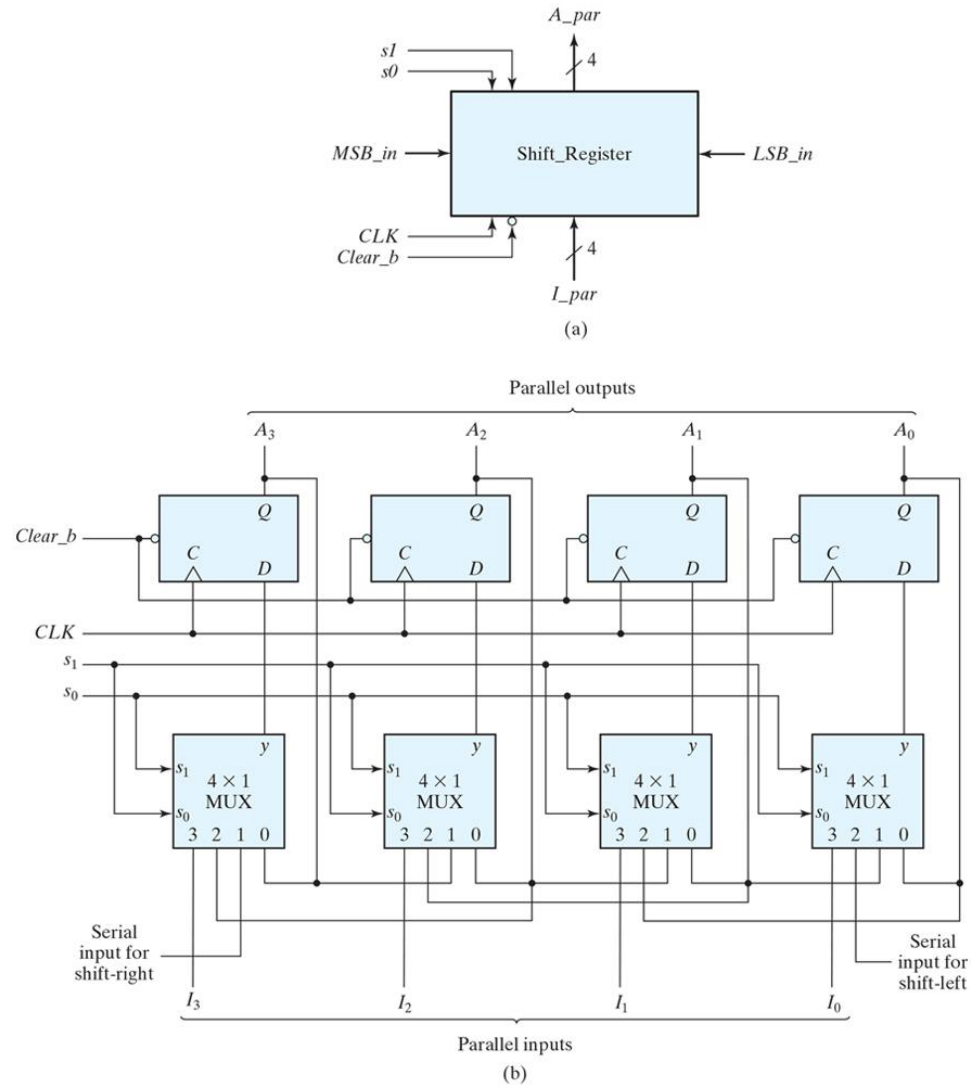


**Table 6.3**

**Function Table for the Register of Fig. 6.7.**

<b>Mode Control</b>		<b>Register Operation</b>
<b><math>s_1</math></b>	<b><math>s_0</math></b>	
0	0	No change
0	1	Shift right
1	0	Shift left
1	1	Parallel load


**Figure 6.8**  
**Four-bit binary ripple counter.**

 


**Table 6.4**  
**Binary Count Sequence.**

$A_3$	$A_2$	$A_1$	$A_0$
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0

**Figure 6.9**  
**State diagram of a decimal BCD counter.**

 


**Figure 6.10**  
**BCD ripple counter.**

 





**Figure 6.11**  
**Block diagram of a three-decade decimal BCD counter.**

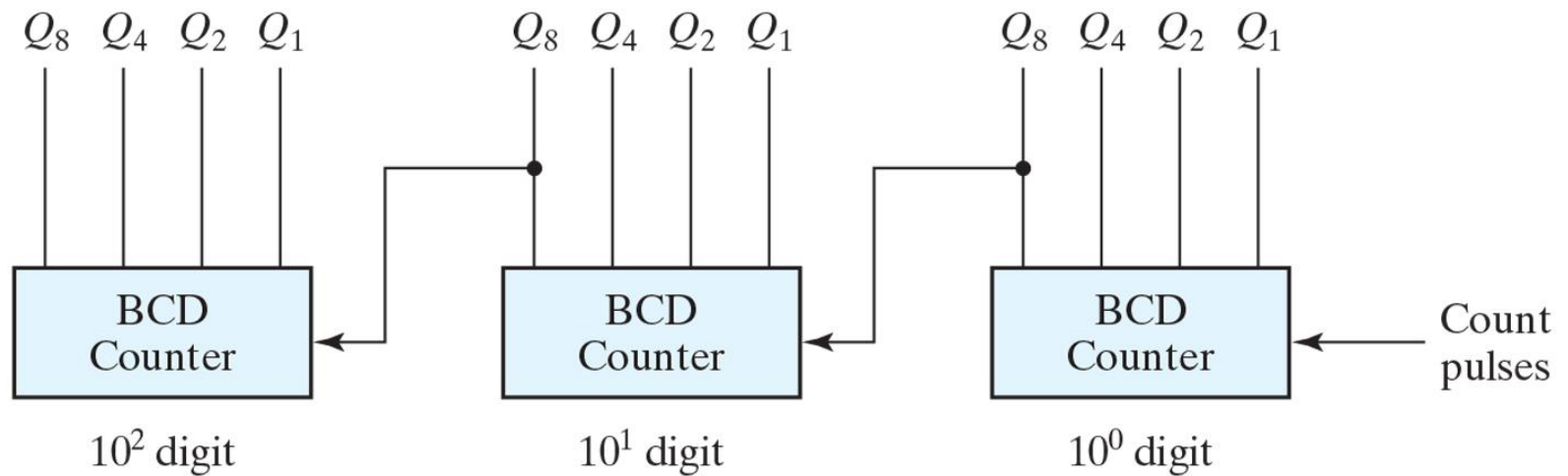

**Figure 6.12**  
**Four-bit synchronous binary counter.**

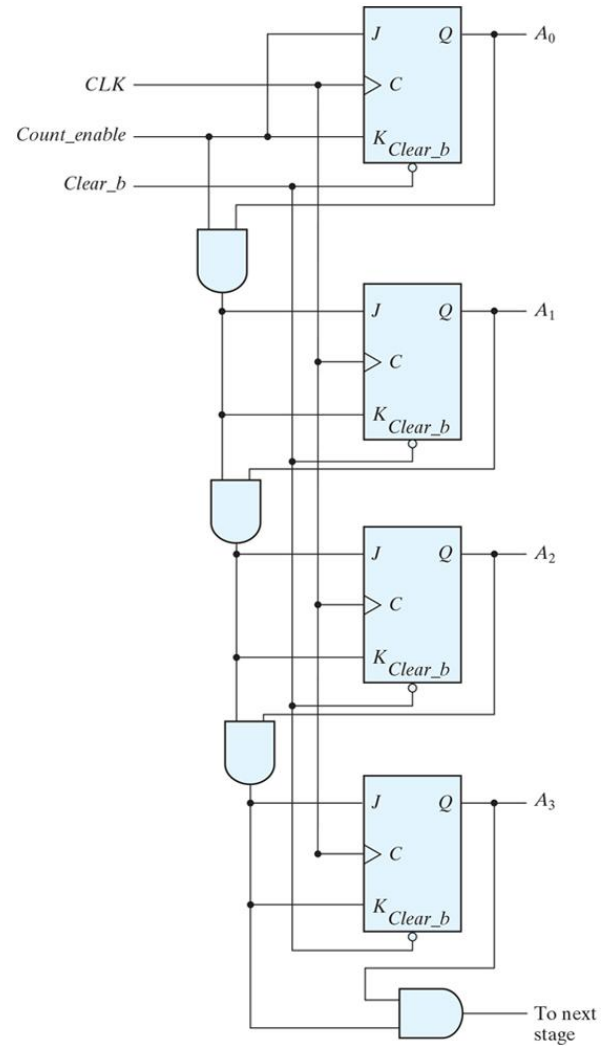


**Figure 6.13**  
**Four-bit up–down binary counter.**

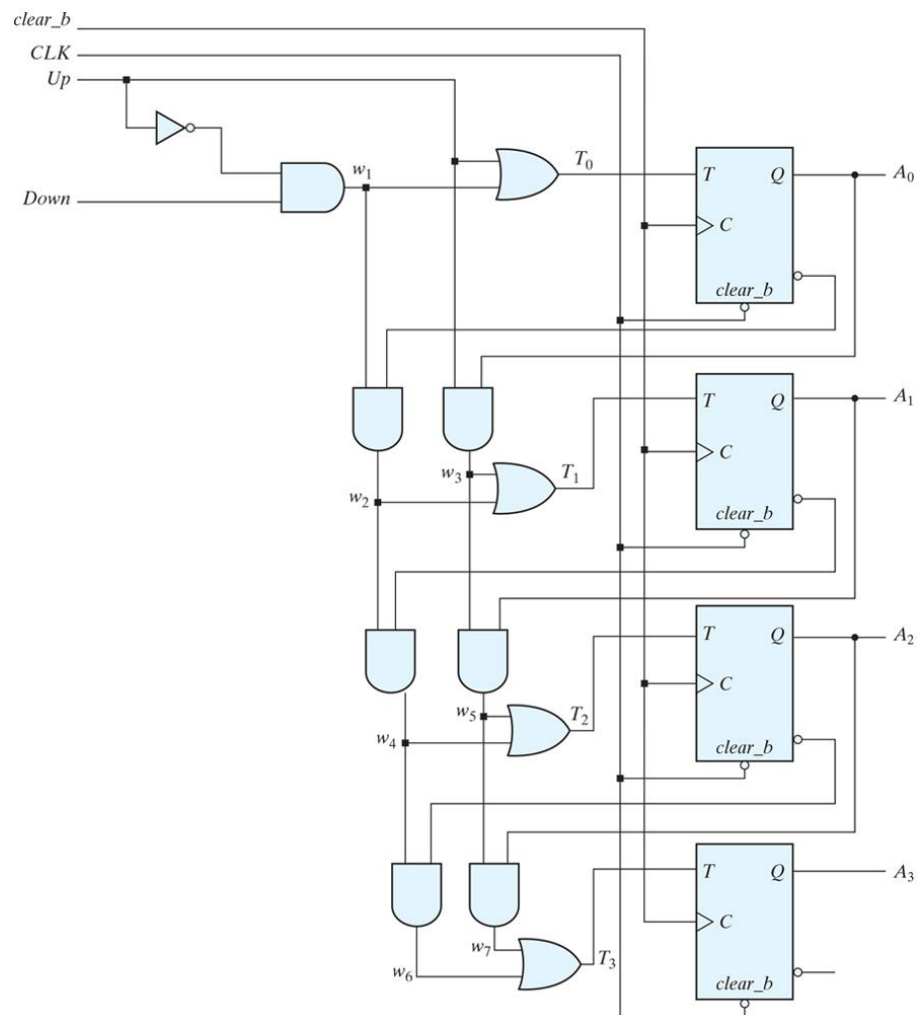

**Table 6.5**  
**State Table for BCD Counter.**

Present State				Next State				Output	Flip-Flop Inputs			
$Q_8$	$Q_4$	$Q_2$	$Q_1$	$Q_8$	$Q_4$	$Q_2$	$Q_1$	$y$	$T_{Q8}$	$T_{Q4}$	$T_{Q2}$	$T_{Q1}$
0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	1	0	0	1	0	0	0	0	1	1
0	0	1	0	0	0	1	1	0	0	0	0	1
0	0	1	1	0	1	0	0	0	0	1	1	1
0	1	0	0	0	1	0	1	0	0	0	0	1
0	1	0	1	0	1	1	0	0	0	0	1	1
0	1	1	0	0	1	1	1	0	0	0	0	1
0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	0	0	1	0	0	0	0	1
1	0	0	1	0	0	0	0	1	1	0	0	1

**Figure 6.14**  
**Four-bit binary counter with parallel load.**

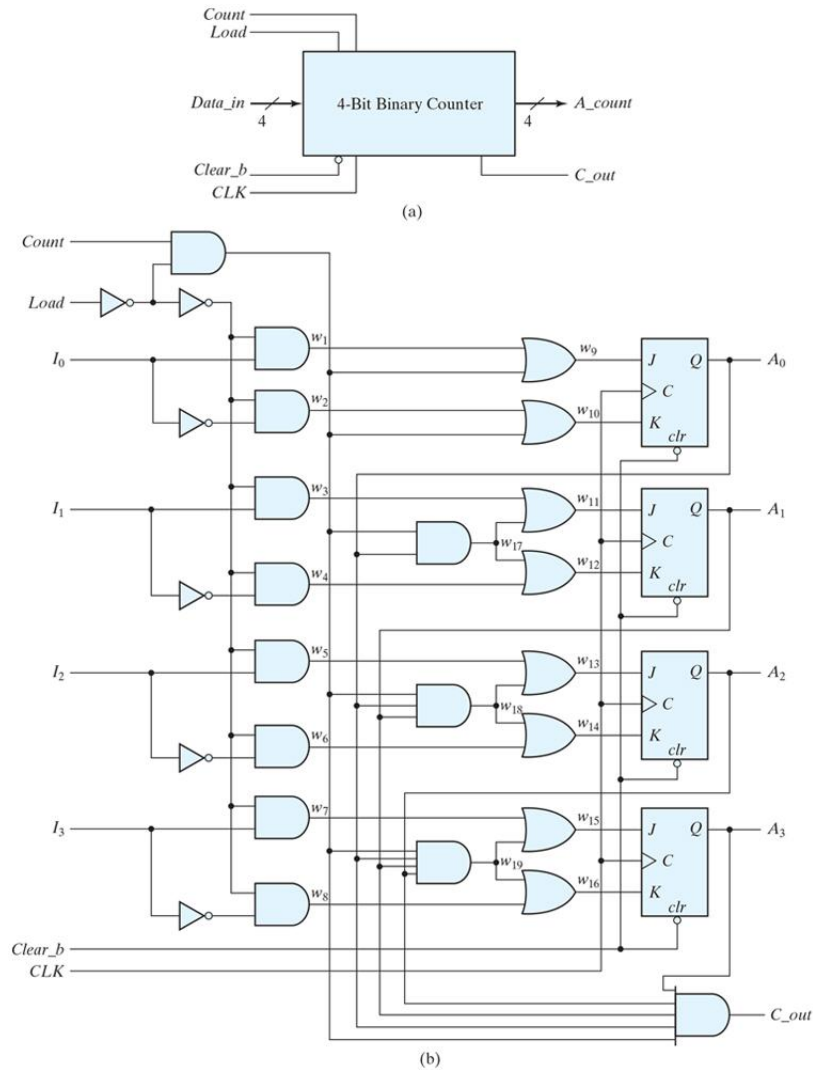


**Table 6.6**

**Function Table for the Counter of Fig. 6.14.**


<b>Clear_b</b>	<b>CLK</b>	<b>Load</b>	<b>Count</b>	<b>Function</b>
0	X	X	X	Clear to 0
1	↑	1	X	Load inputs
1	↑	0	1	Count next binary state
1	↑	0	0	No change

## Figure 6.15
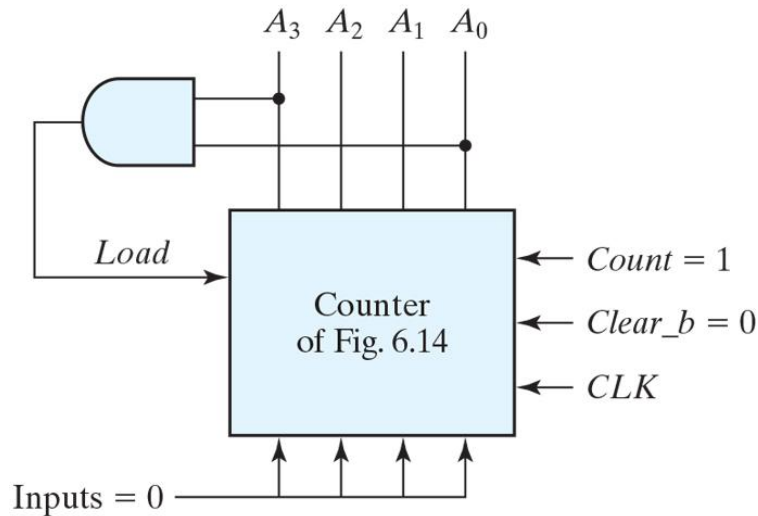
### Two ways to achieve a BCD counter using a counter with parallel load.



(a) Using the load input

 

(b) Using the clear input

**Table 6.7**  
**State Table for Counter.**

Present State			Next State			Flip-Flop Inputs					
<i>A</i>	<i>B</i>	<i>C</i>	<i>A</i>	<i>B</i>	<i>C</i>	<i>J<sub>A</sub></i>	<i>K<sub>A</sub></i>	<i>J<sub>B</sub></i>	<i>K<sub>B</sub></i>	<i>J<sub>C</sub></i>	<i>K<sub>C</sub></i>
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	1	0	0	1	X	X	1	0	X
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	0	0	0	X	1	X	1	0	X



Figure 6.16  
Counter with unused states.

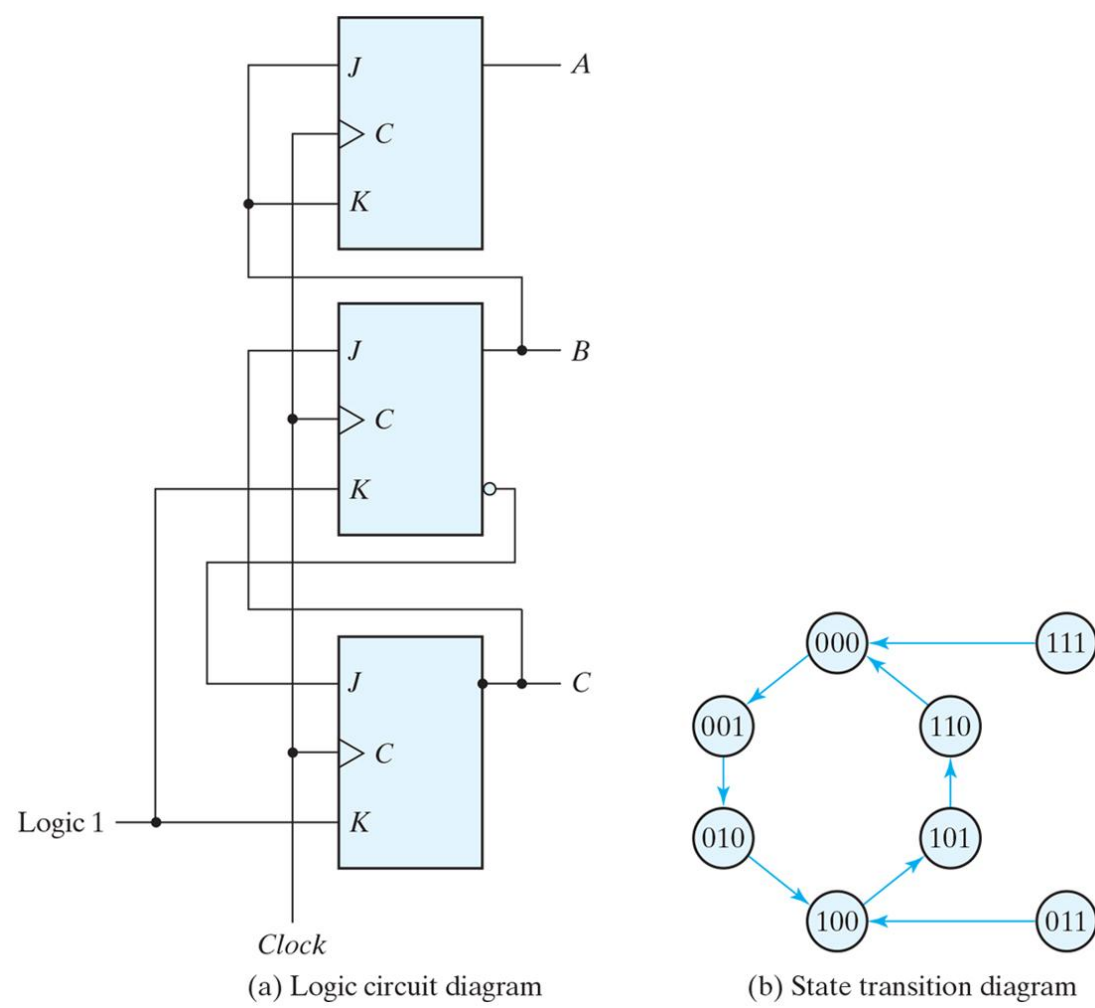


Figure 6.17  
Generation of timing signals.


 




Figure 6.18  
Construction of a Johnson counter.

 

Sequence number	Flip-flop outputs				AND gate required for output
	A	B	C	E	
1	0	0	0	0	$A'E'$
2	1	0	0	0	$AB'$
3	1	1	0	0	$BC'$
4	1	1	1	0	$CE'$
5	1	1	1	1	$AE$
6	0	1	1	1	$A'B$
7	0	0	1	1	$B'C$
8	0	0	0	1	$C'E$

(b) Count sequence and required decoding


**Figure 6.19**  
**Simulation output of HDL Example 6.4.**

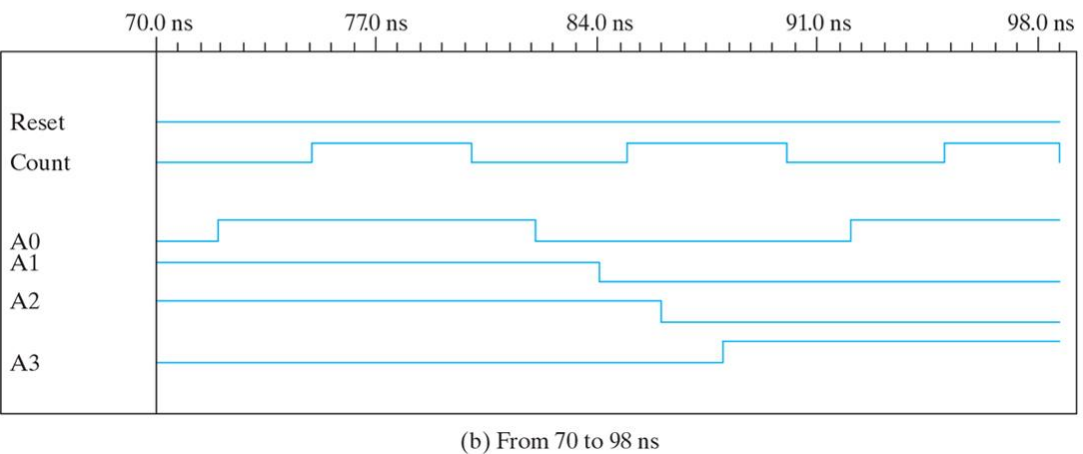 

## Problem 6.7

$s_1$	$s_0$	Register Operation
0	0	No change
1	0	Complement the four outputs
0	1	Clear register to 0 (synchronous with the clock)
1	1	Load parallel data

Figure P6.21

 

**Figure P6.47**  
**Circuit for Problem 6.47.**

 


Figure P6.48  
Circuit for Problem 6.48.

